

# **Digital Design and Computer Organization Laboratory**

**UE19CS206**

**3<sup>rd</sup> Semester, Academic Year 2020-21**

Date : 01-10-2020

Name: Suhan.B.Revankar	SRN: PES2UG19CS412	Section: G
---------------------------	-----------------------	---------------

Week# \_\_4\_\_

Program Number : \_\_1\_\_

Title of the Program

## **REGISTER FILE**

**AIM: TO CONSTRUCT A REGISTER FILE, FROM WHICH TWO 16-BIT VALUES CAN BE READ, AND TO WHICH ONE 16-BIT VALUE WRITTEN, EVERY CLOCK CYCLE.**

1: Paste the Screen Shot of the source code in reg file.v

```
reg_file - Notepad
File Edit Format View Help

// Write code for modules you need here

module dfri_16 (input wire clk, reset, load, input wire [15:0] in, output wire [15:0] out);
dfri_f0(clk,reset,load,in[0],out[0]);
dfri_f1(clk,reset,load,in[1],out[1]);
dfri_f2(clk,reset,load,in[2],out[2]);
dfri_f3(clk,reset,load,in[3],out[3]);
dfri_f4(clk,reset,load,in[4],out[4]);
dfri_f5(clk,reset,load,in[5],out[5]);dfri_f6(clk,reset,load,in[6],out[6]);
dfri_f7(clk,reset,load,in[7],out[7]);
dfri_f8(clk,reset,load,in[8],out[8]);
dfri_f9(clk,reset,load,in[9],out[9]);
dfri_f10(clk,reset,load,in[10],out[10]);
dfri_f11(clk,reset,load,in[11],out[11]);
dfri_f12(clk,reset,load,in[12],out[12]);
dfri_f13(clk,reset,load,in[13],out[13]);
dfri_f14(clk,reset,load,in[14],out[14]);
dfri_f15(clk,reset,load,in[15],out[15]);
endmodule

module mux8_16 (input wire [0:15] i0, i1, i2, i3, i4, i5, i6, i7, input wire [0:2] j,
output wire [0:15] o);
mux8 mux8_0({i0[0], i1[0], i2[0], i3[0], i4[0], i5[0], i6[0], i7[0]}, j[0], j[1], j[2], o[0]);
mux8 mux8_1({i0[1], i1[1], i2[1], i3[1], i4[1], i5[1], i6[1], i7[1]}, j[0], j[1], j[2], o[1]);
mux8 mux8_2({i0[2], i1[2], i2[2], i3[2], i4[2], i5[2], i6[2], i7[2]}, j[0], j[1], j[2], o[2]);
mux8 mux8_3({i0[3], i1[3], i2[3], i3[3], i4[3], i5[3], i6[3], i7[3]}, j[0], j[1], j[2], o[3]);
mux8 mux8_4({i0[4], i1[4], i2[4], i3[4], i4[4], i5[4], i6[4], i7[4]}, j[0], j[1], j[2], o[4]);
mux8 mux8_5({i0[5], i1[5], i2[5], i3[5], i4[5], i5[5], i6[5], i7[5]}, j[0], j[1], j[2], o[5]);
mux8 mux8_6({i0[6], i1[6], i2[6], i3[6], i4[6], i5[6], i6[6], i7[6]}, j[0], j[1], j[2], o[6]);
mux8 mux8_7({i0[7], i1[7], i2[7], i3[7], i4[7], i5[7], i6[7], i7[7]}, j[0], j[1], j[2], o[7]);
mux8 mux8_8({i0[8], i1[8], i2[8], i3[8], i4[8], i5[8], i6[8], i7[8]}, j[0], j[1], j[2], o[8]);
mux8 mux8_9({i0[9], i1[9], i2[9], i3[9], i4[9], i5[9], i6[9], i7[9]}, j[0], j[1], j[2], o[9]);
mux8 mux8_10({i0[10], i1[10], i2[10], i3[10], i4[10], i5[10], i6[10], i7[10]}, j[0], j[1], j[2], o[10]);
mux8 mux8_11({i0[11], i1[11], i2[11], i3[11], i4[11], i5[11], i6[11], i7[11]}, j[0], j[1], j[2], o[11]);
mux8 mux8_12({i0[12], i1[12], i2[12], i3[12], i4[12], i5[12], i6[12], i7[12]}, j[0], j[1], j[2], o[12]);
mux8 mux8_13({i0[13], i1[13], i2[13], i3[13], i4[13], i5[13], i6[13], i7[13]}, j[0], j[1], j[2], o[13]);
mux8 mux8_14({i0[14], i1[14], i2[14], i3[14], i4[14], i5[14], i6[14], i7[14]}, j[0], j[1], j[2], o[14]);
mux8 mux8_15({i0[15], i1[15], i2[15], i3[15], i4[15], i5[15], i6[15], i7[15]}, j[0], j[1], j[2], o[15]);
endmodule

module reg_file (input wire clk, reset, wr, input wire [0:2] rd_addr_a,
rd_addr_b, wr_addr, input wire [0:15] d_in,
output wire [0:15] d_out_a, d_out_b);
wire [0:7] load;
wire [0:15] dout_0, dout_1, dout_2, dout_3, dout_4, dout_5, dout_6, dout_7;
dfri_16 dfri_16_0(clk,reset,load[0],d_in,dout_0);
dfri_16 dfri_16_1(clk,reset,load[1],d_in,dout_1);
dfri_16 dfri_16_2(clk,reset,load[2],d_in,dout_2);
dfri_16 dfri_16_3(clk,reset,load[3],d_in,dout_3);
dfri_16 dfri_16_4(clk,reset,load[4],d_in,dout_4);
dfri_16 dfri_16_5(clk,reset,load[5],d_in,dout_5);
dfri_16 dfri_16_6(clk,reset,load[6],d_in,dout_6);
dfri_16 dfri_16_7(clk,reset,load[7],d_in,dout_7);
demux8 demux8_0(wr,wr_addr[2],wr_addr[1],wr_addr[0],load);
mux8_16 mux8_16_9(dout_0, dout_1, dout_2, dout_3, dout_4, dout_5, dout_6, dout_7, rd_addr_a, d_out_a);
mux8_16 mux8_16_10(dout_0, dout_1, dout_2, dout_3, dout_4, dout_5, dout_6, dout_7, rd_addr_b, d_out_b);
endmodule
```

## 2. Complete the truth table for all the 6 rows

The first four combinations that implement write operation and the last two combinations that implement read operation.


wr	rd_addr_a				rd_addr_b				wr_addr			d_in	Output
25	24	23	22	21	20	19	18	17	16	Bit15 to Bit 0			
1	x	x	x	x	x	x	0	1	1	CDEF	Reg3=CDEF		
1	x	x	x	x	x	x	1	1	1	3210	Reg7=3210		
1	0	1	1	1	1	1	1	0	1	4567	Reg5=4567		
1	0	0	1	1	0	1	0	0	0	BA98	Reg0=BA98		
0	0	0	1	1	0	1	0	0	1	xxxx	d_out_a=0000 d_out_b=4567		
0	0	0	0	0	0	0	x	x	x	xxxx	d_out_a=BA98 d_out_b=BA98		

### 3: Paste the Screen shot of the GTKWave form

#### I. SCREENSHOT1
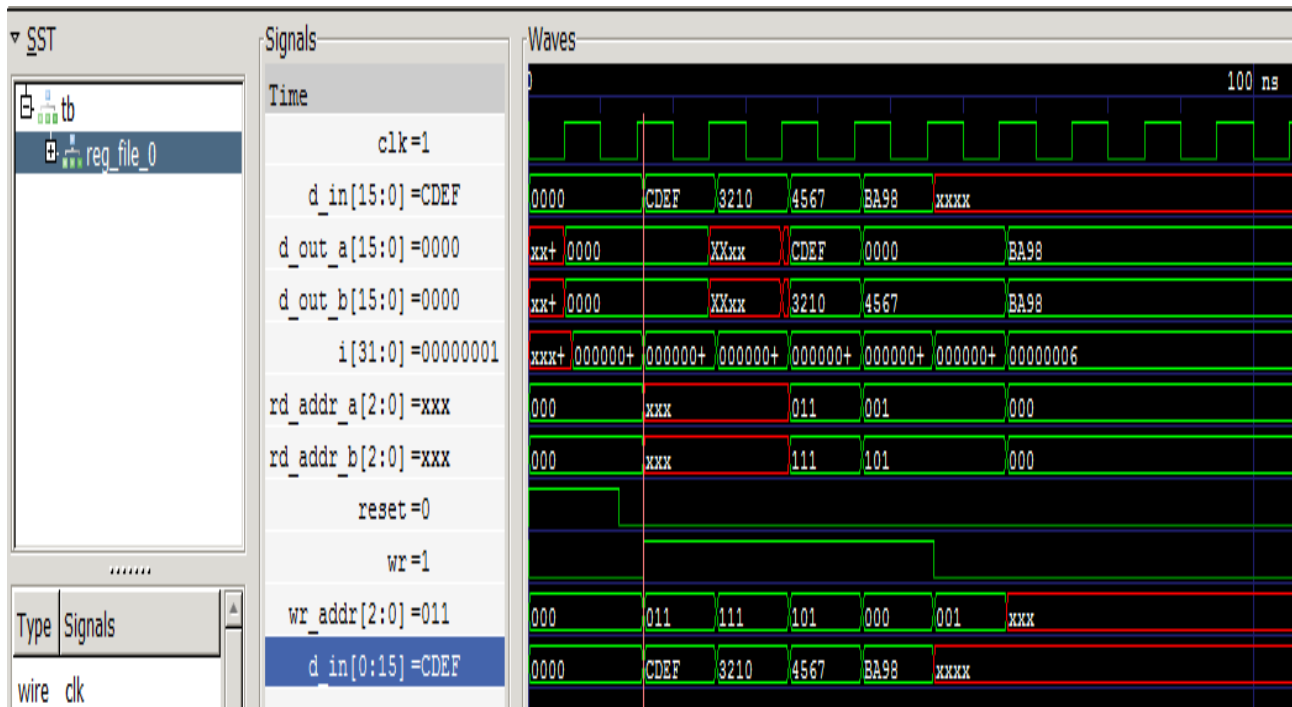
##### **CASE1 (Write operation):**


wr=1 ,Write Address=011,d\_in=CDEF,Verify in[15:0] of Register 3



#### II. SCREENSHOT 2
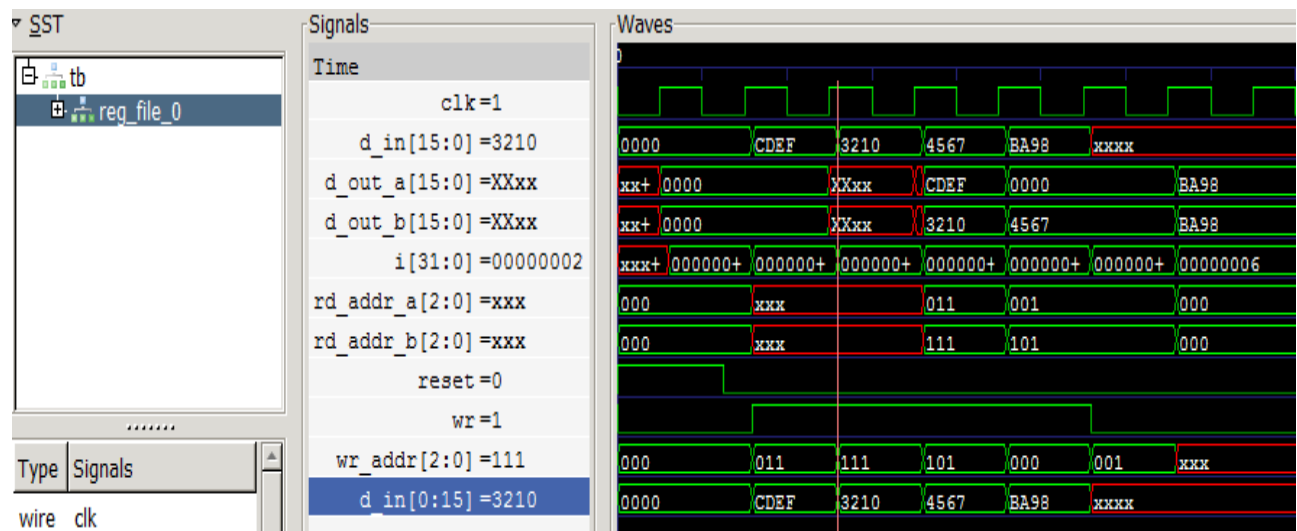
##### **CASE2 (Write operation):**


wr=1 ,Write Address=111,d\_in=3210,Verify in[15:0] of Register 7



### III. SCREENSHOT 3
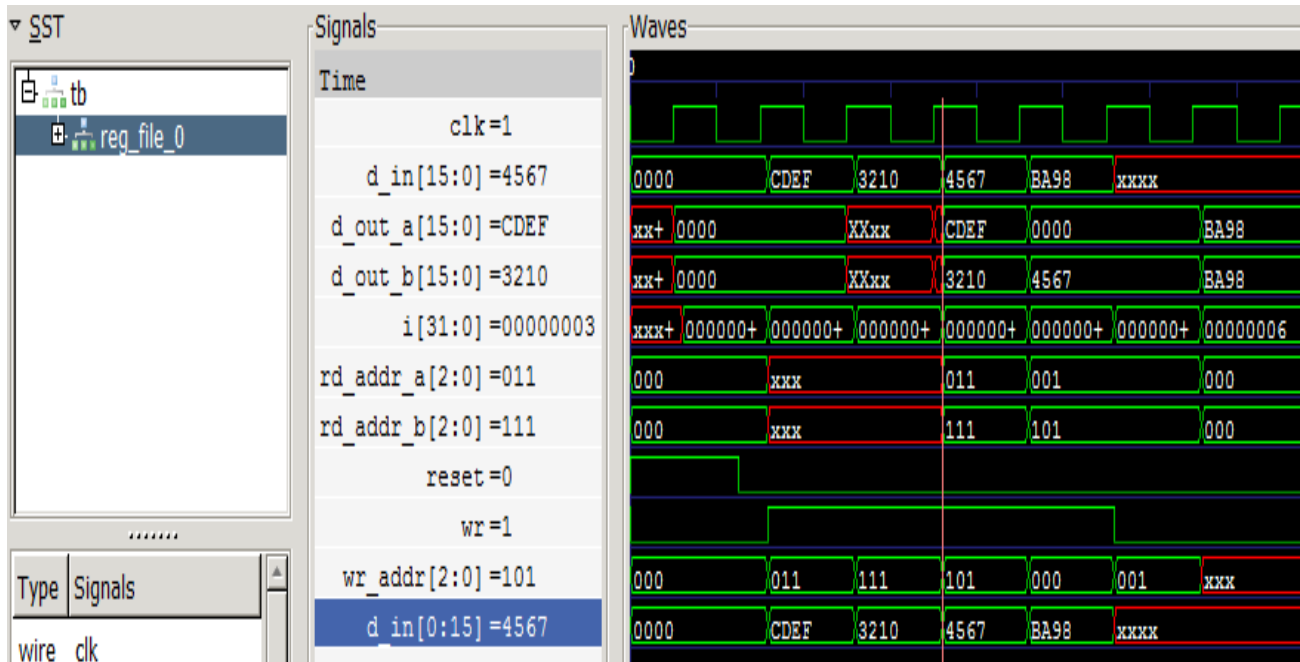
#### CASE 3 (Write operation):


wr=1 ,rd\_addr\_a=011, rd\_addr\_b=111,wr\_addr=101,  
d\_in=4567,Verify in[15:0] of Register 5



### iv. SCREENSHOT 4

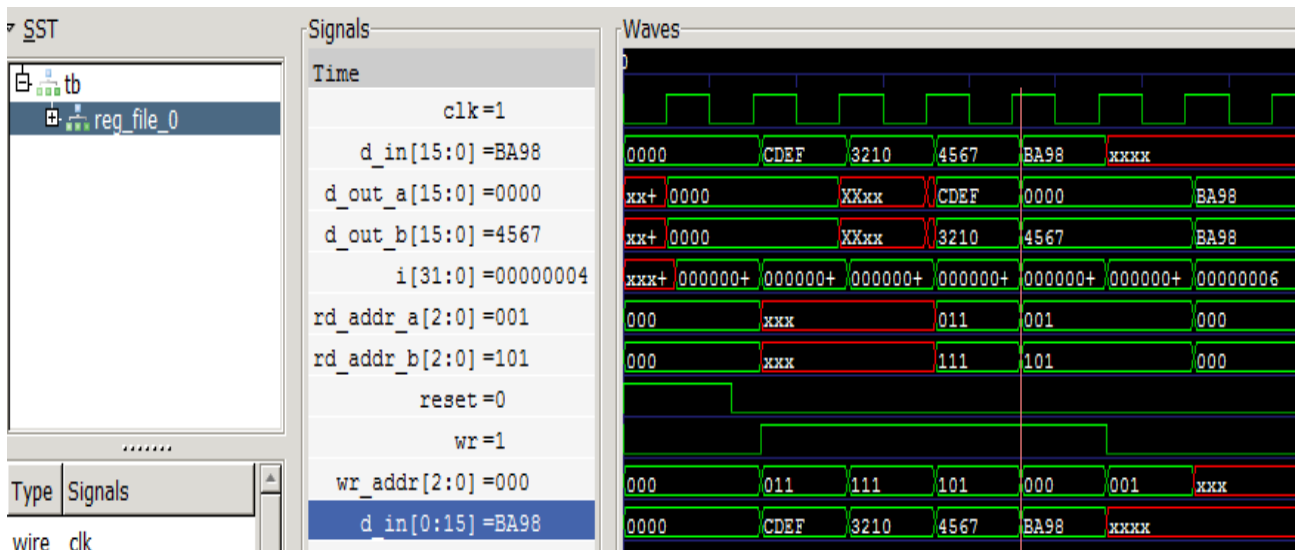
#### CASE 4 (Write operation):

wr=1 ,rd\_addr\_a=001, rd\_addr\_b=101,wr\_addr=000,  
d\_in=BA98,Verify in[15:0] of Register 0



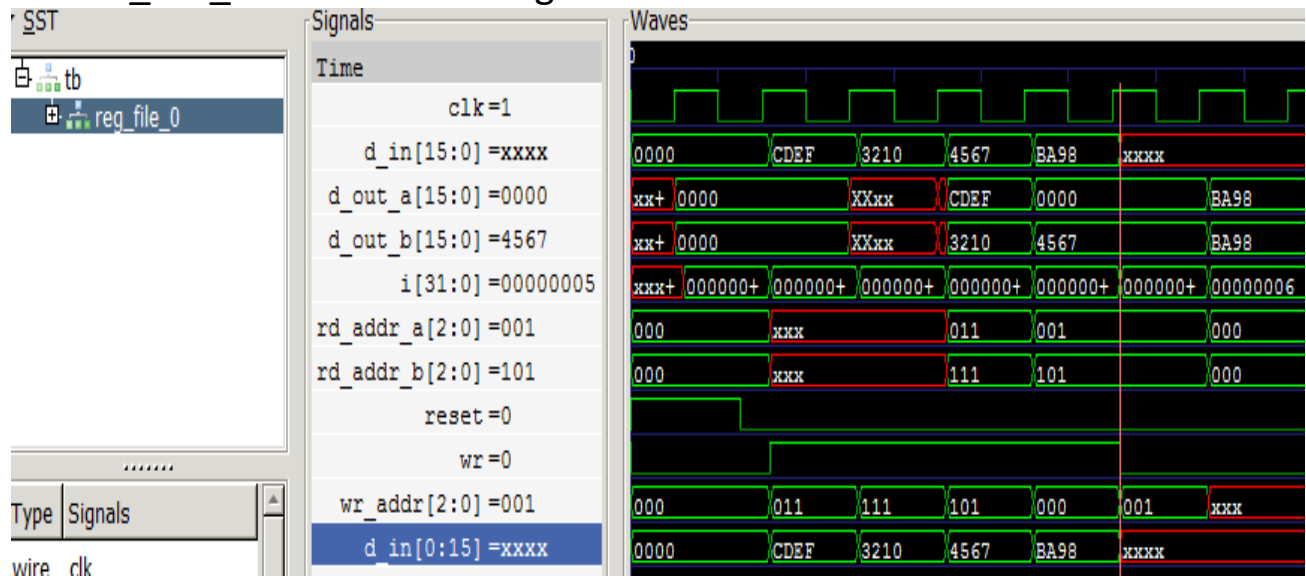
v. SCREENSHOT 5 **CASE 5 (Read operation):**

wr=0 , rd\_addr\_a=001, rd\_addr\_b=101,wr\_addr=001,  
Verify d\_out\_a=Content of Register 1,  
d\_out\_b==Content of Register 5



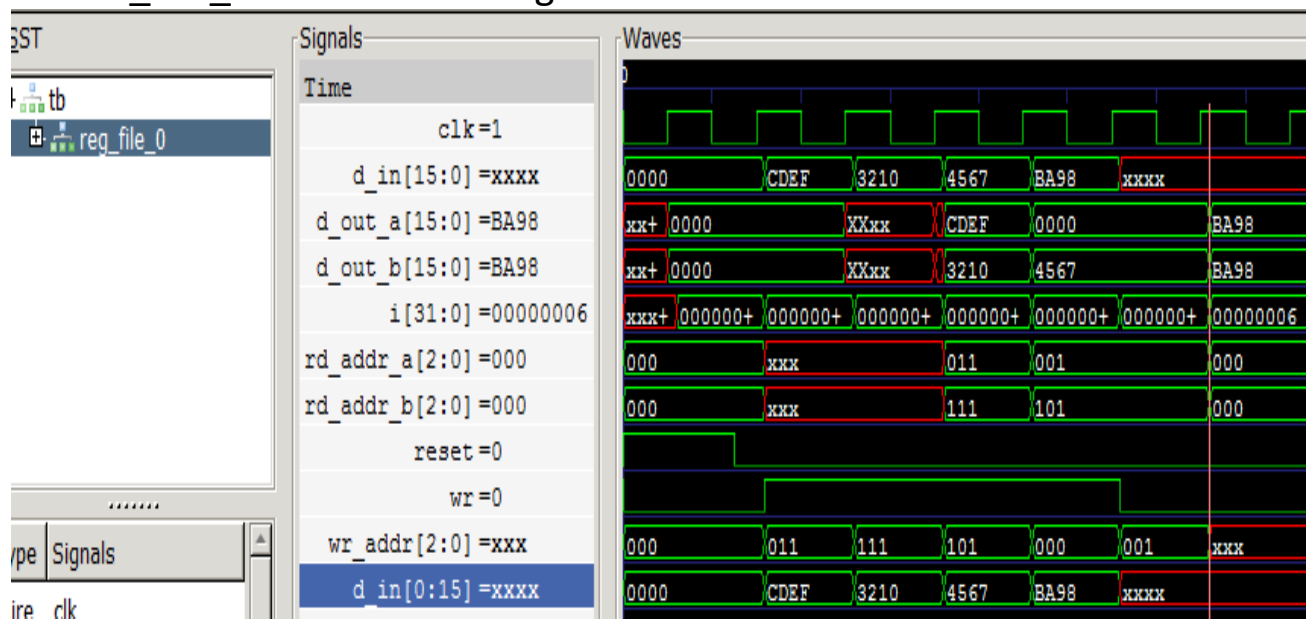vi. SCREENSHOT 6 **CASE 6 (Read operation):**

wr=0 , rd\_addr\_a=000, rd\_addr\_b=000,wr\_addr= XXXX  
Verify d\_out\_a=Content of Register 0,  
d\_out\_b==Content of Register 0



### **Disclaimer:**

- The programs and output submitted is duly written, verified and executed by me.
- I have not copied from any of my peers nor from the external resource such as internet.
- If found plagiarized, I will abide with the disciplinary action of the University.

Signature :

Suhan.B.Revankar

Name : Suhan.B.Revankar

SRN:PES2UG19CS412

Section : G

Date : 01-10-2020